Tutorial exercise Chapter 4- Node voltage analysis

Pre-questions:

Q1) What is the course code and course name?

Q2) What are the learning objectives of this course?


Q3) There are two course learning outcomes. Name one of it.

Q4) What are the assessment methods in this course? Please table it and sum to 100%.

Question 1


Solve the question :

a) Write the network equations
b) Put the network equations into standard form and matrix form
c) Solve for V1, V2, V3.

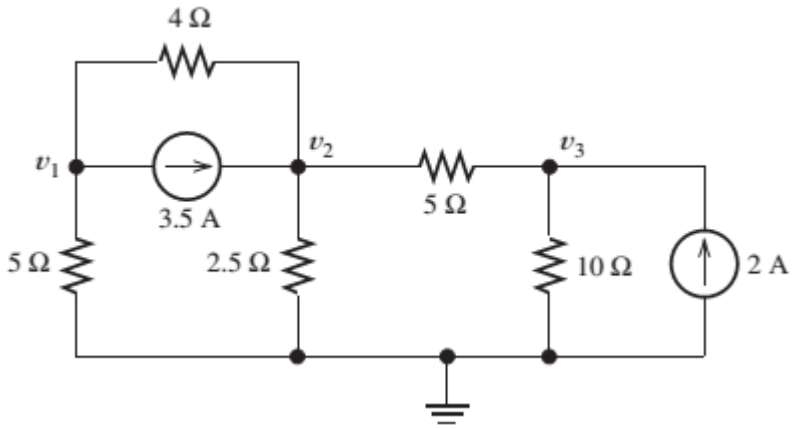

Question 2


Solve for node voltages V1 and V2 using node-voltage analysis.

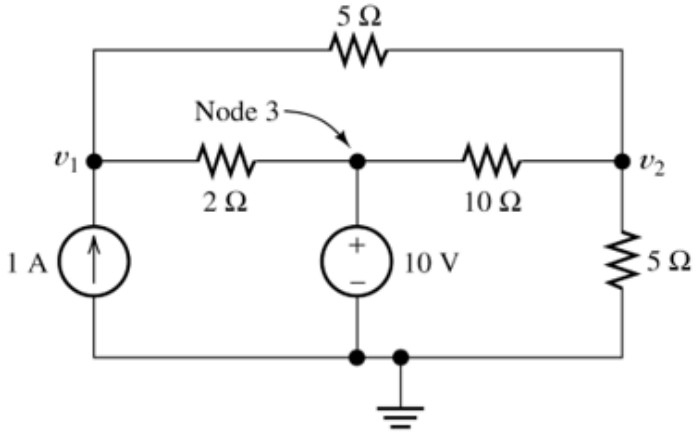

Question 3

Solve for node voltages v1 and v2 using node-voltage analysis.

d) Write the network equations
e) Solve for V1, V2.

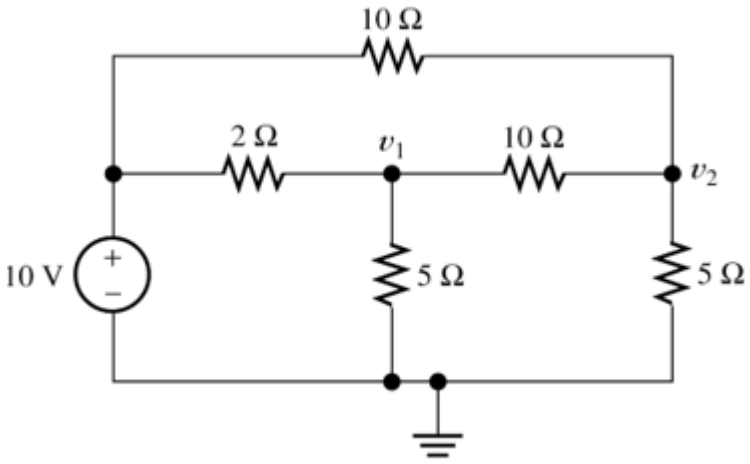

Question 4

Write a set of network equations for the node voltages.

