
Tutorial Exercise: Chapter 6 (Part 1)


Question 1:

Find the Thevenin resistance for each of the circuits by zeroing the sources.

(a)

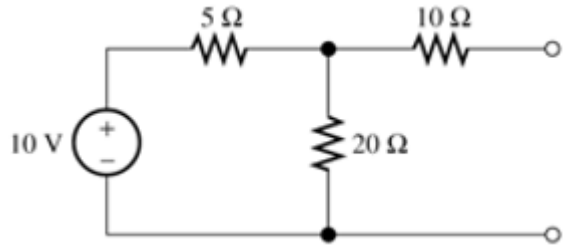

(b)

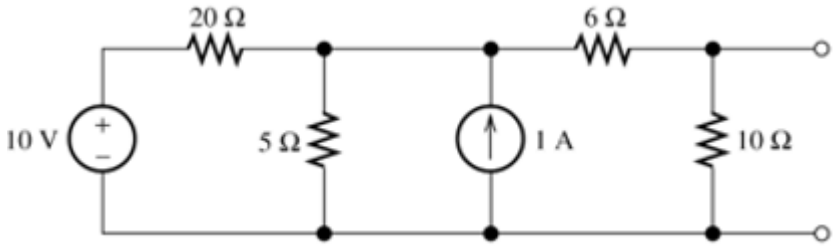

Question 2

(a) Find the Thevenin equivalent for the circuit shown below.
(b) Find the Norton equivalent for the circuit shown below.

