

Tutorial Chapter 3

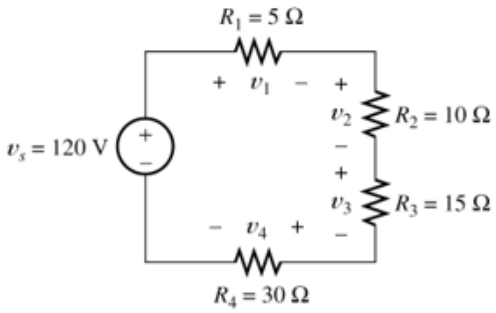Question 1: Find all the voltages in Figure (a) and Figure (b).




(a)

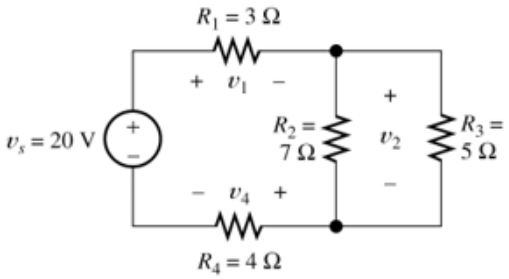


(b)

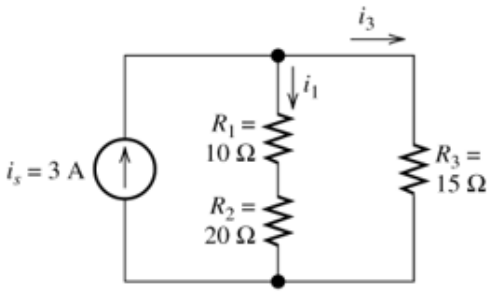Question 2: Find all the current in Figure (a) and (b).




(a)

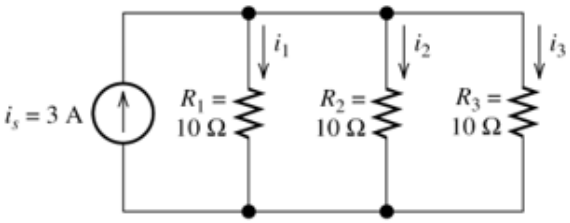


(b)

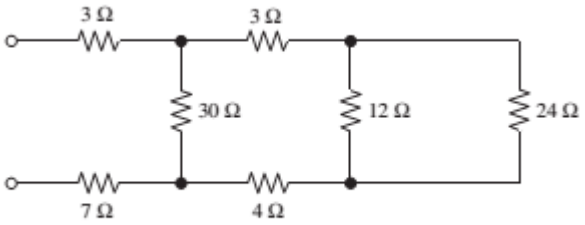Question 3: Reduce the network diagram to a single equivalent resistance by combining them in series and parallel, for Figure (a) and (b).



(a)

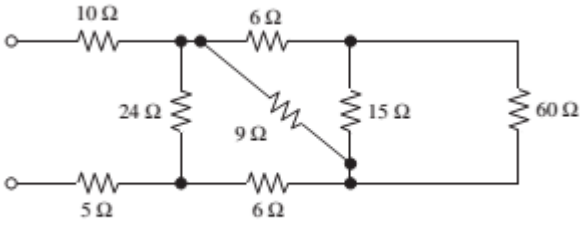

(b)