
Exercise Chapter 7


Question 1:

Use source transformations to solve for the values i_1 and i_2 for the circuit below.

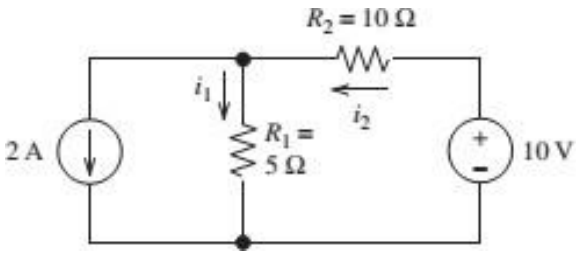

Question 2:

Find the load resistance for maximum power transfer from the circuit. Also, find the maximum power.

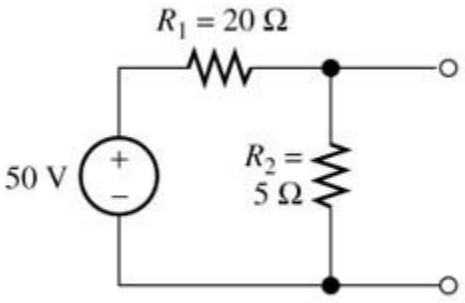

Question 3

Use superposition to find the responses V_T and i_T for the circuit below.

