
Chapter 5 Mesh Analysis Tutorial

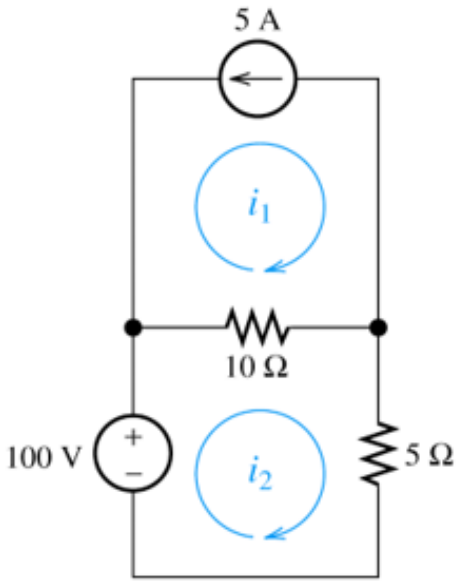Q1. Write the equations needed to solve for the mesh currents.



Q2 Write the equations needed to solve for the mesh currents.

